



Fig. 2: Inside the cascode preselector. The two BNCs at the rear are for the antenna and radio.

transistor circuit where each transistor amplifies the signal in a slightly different circuit configuration, together creating a more versatile amplifier. A conventional common base transistor amplifier, for example, has a wideband response but unfortunately it has a low input impedance that limits its application. If we start with a common emitter amplifier but follow it with the common base circuit, we can create a circuit that has a wideband amplifier with high input impedance. The stages are in cascode, that is to say, stacked 'above' one another in series rather than in cascade ('behind' one another) as in a standard amplifier chain.

Developed in the 1930s, the cascode name is derived from its initial application to create a pentode circuit from two triodes: "*CASCade triodes having similar characteristics to a pentODE*". The arrangement produces high gain along with wideband high frequency response. There is also little internal coupling between the input and output so the circuit is very stable. This circuit is often used in transceiver designs to create high performance, high gain mixers. Note, though, that a standard dual-gate MOSFET preamplifier is a sort of simplified cascode amplifier but has lower gain and less input/output isolation than a two-transistor cascode circuit.

80m Band Cascode Preselector

The 80m cascode preselector described here provides a much-needed bit of RF gain to my homemade direct conversion receiver. The first stage of our FET cascode amplifier is a common source amplifier followed by a second stage with a common gate configuration. The first provides a high input impedance and gain while the second stage provides buffering (isolation) between input and output along with good bandwidth. I have chosen 80m band coils but the circuit will, of course, work well for other bands with suitable tuning coils.

The Circuit

The circuit diagram is shown at **Fig. 1**. The two transistors in the cascode need to have similar specifications. I used a U257 (bought on eBay) that contains two matched FETs in one device. I used two commercially made tuned circuits for the amplifier (the same inductors as used in the RSGB 80m band PSK centenary receiver – 45 μ H, from Spectrum Communications) but you could wind your own (and coils for other bands). I made my preselector for the SSB DX end of 80m (3.7 to 3.8 MHz) so you could simply rely on the ferrite tuning core slugs to tune the preamplifier. However, I also included a two-gang low capacitance tuning capacitor (50+50pF or so). Each

gang was wired to one of the tuned circuits so that I could peak for maximum gain (the common is wired to earth/case). If you want to cover a greater range of frequencies, you can use a larger value dual-gang capacitor.

Because the cascode circuit is very stable, the layout for the 80m band preselector is not very critical. As with all amplifiers, you should try to keep all the component leads as short as possible and keep the input away from the output. Finally, because the transistors are effectively in cascade series across the supply, a higher than normal voltage is required, for example 2 x 9V = 18V instead of 9V. I used a wafer switch to bypass the preselector when not wanted and also to switch the power on/off.

The photograph, **Fig. 2**, shows the internal layout that I used.

Setting Up

Once you have double-checked all the components and their orientation, apply 18V and measure the current flowing into the circuit. If all is well, it will only be about 10mA. Connect an antenna to the input and the cascode output to the receiver. Tune the radio to the part of the band you want to focus on (in my case 3.75 to 3.80MHz) and set the tuning capacitor to midway. Now adjust the tuning cores for maximum signal at the radio.



Fig. 3: The cascode preselector (left) installed next to my homemade direct conversion receiver (right). The large knob on the preselector is the tuning capacitor while the smaller knob turns the power on/off and bypasses the unit.

Note that the ferrite tuning slugs in the two coils may not peak at exactly the same position on the two coils (this is normal). If you move frequency a little, the dual tuning capacitor should allow peaking of the cascode amplifier. I used BNC sockets for input and output. Unless you have the correct D-shaped hole punch to make the correct holes, I recommend you use four bolt hole BNC sockets. The nut fixed sockets always become loose after a while and are a nuisance.

preselector for many years and found it to be effective but the cascode amplifier described here is better. I have made a short video on my YouTube channel that shows a very simple audio test that compares the two preselectors side by side, switching them in and out of circuit so you can hear the improvement and compare results.

The photograph, **Fig. 3**, shows the assembled preselector in use next to my homebrew direct conversion receiver.

videos on (i) tackling noise on the shortwave bands and (ii) for a simple audio test comparing a single FET with the cascode preselector: search "jonathan hare + 80m band" on YouTube.

Updates and additions to this project can be found on my website:

www.creative-science.org.uk/g1exg.html
Jonathan's YouTube channel can also be found at the following URL:
www.youtube.com/channel/UCwAIQLexP-274212Tnfz9sg

Results

I have been using a single FET 2N3819

Links

Please visit my YouTube channel for

Radio Book Store

See page 72 or order securely online at www.pwpublishing.ltd.uk

CARRYING ON THE PRACTICAL WAY. £14.99 20 YEARS OF PROJECTS IN PRACTICAL WIRELESS

Since 1996 there has been an on-going series of small practical projects in the *Practical Wireless* magazine. The Rev. George Dobbs G3RJV has been the mainstay of this series by far, having written around 95% of the articles that appeared up to date. So, as a tribute to George's love of the hobby and to the other authors who take over the task of demonstrating that building your own projects is easier than you might think, we've collated them into one electronic archive.

Because of the wide-ranging subjects it's not easy to catalogue them, as there are around 230 articles to browse through. Some of necessity are similar in nature, but all are unique in showing how easy it can be to create small circuits that can be coupled together to produce receivers, transmitters, test equipment or just plain novelties to amuse. But all are part of the self-training aspect of the hobby.

