


5

OSCILLATOR

LM 3909

completed flashing circuit

(made) 21/2/80

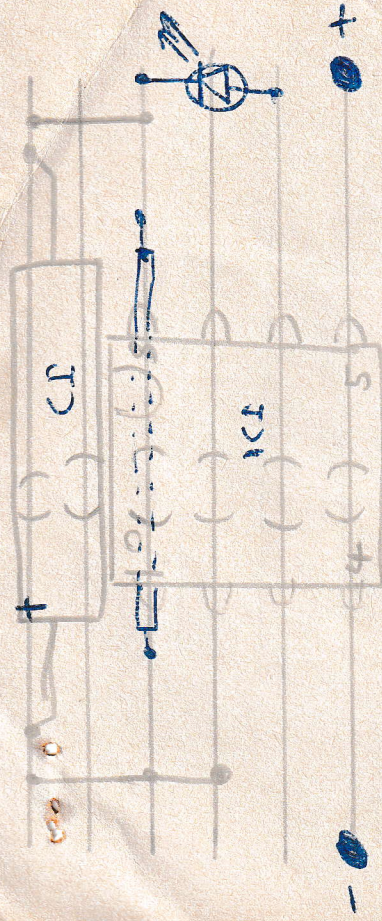

$\square = \text{Wave Drink}$

This device is designed specifically to flash light emitting diodes. (Led) By using a timing capacitor a voltage in excess of 2 volts is applied to the Led while operating on a 1.5v supply.

This = 24/12/20 4


Chip Led Flasher

OSCILLATOR

LM3909

complete flashing circuit

(made # 21/2/20)

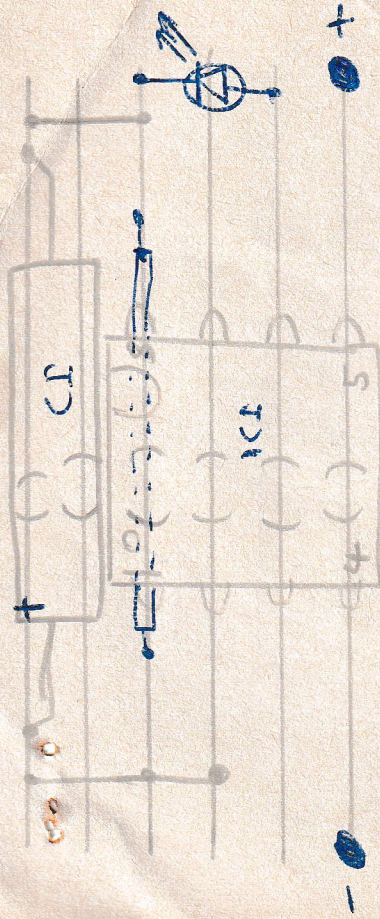

$\square$ = Wave Link

This device is designed specifically to flash light emitting diodes (Leds). By using a timing capacitor a voltage in excess of 2 volts is applied to the Led while operating on a 1.5v supply.